

## Big Ideas

---

- Electricity consists of charged particles moving in a continuous circuit
- Voltage, Current, and Resistance are related to each other through Ohm's Law
- The total current flowing into a junction must equal the total current flowing out of that same junction
- The voltage dropped around a continuous loop traced in a circuit must equal the voltage provided
- Resistors can be combined in different ways to produce different results
- It is possible that the act of taking a measurement will change the value being measured
- The resistance of a wire is affected by its thickness, length, and material resistivity
- Many applications use a potential divider circuit design to produce a result when certain conditions are met
- The voltage that a battery can supply is related to its internal resistance

## Content Objectives

---

### 8.1 – Electrical Current

 p. 208-213, 217-218

I can quantify charge in terms of Coulombs			
I can calculate the charge of a certain # of electrons and the # of electrons for a given charge			
I can describe current in terms of amps and coulombs per second			
I can describe the subatomic properties of a conductor to allow charge to flow			
I can the electron drift speed for a given current and wire			
I can use Kirchoff's First Law to analyze the current flowing in an out of a junction			

### 8.2 – Ohm's Law and Resistance

 p. 219-225

I can use Kirchoff's Second Law to analyze the current flowing in an out of a junction			
I can qualitatively describe voltage, current, and resistance			
I can mathematically relate voltage, current, and resistance using Ohm's Law			
I can describe the difference between ohmic and non-ohmic resistors			
I can identify groups of resistors as being connected in series or parallel			
I can calculate the equivalent resistance for resistors connected in series			
I can calculate the equivalent resistance for resistors connected in parallel			
I can quantitatively describe how adding resistors changes the equivalent resistance			

### 8.3 – Circuits

 p. 226-231

I can calculate the equivalent resistance for resistors in a combination circuit with series AND parallel			
I can describe how voltage is divided across resistors in series			
I can describe how current is divided across parallel branches in a circuit			
I can use a circuit diagram to calculate V, I, and R for resistors in simple series or parallel circuits			
I can use a circuit diagram to calculate V, I, and R for resistors in a combination circuit			

## 8.4 – Measuring Circuits and Resistivity

 p. 226-231

I can explain how a voltmeter or ammeter must be connected in a circuit			
I can identify the resistance required for an ideal voltmeter or ammeter			
I can predict the reading on a meter when given its internal resistance			
I can calculate a meter's internal resistance from a meter reading and circuit diagram			
I can calculate the electrical power of a component when given voltage, current, or resistance			
I can qualitatively describe the factors that affect a wire's resistance			
I can define the resistivity of a meter with proper units			
I can calculate for an unknown variable in the resistivity formula			

## 8.5 – Voltage Dividers and Batteries

 p. 232-241

I can identify the different circuit diagram symbols for different types of resistors			
I can describe how environmental changes can affect the resistance of LDRs and Thermistors			
I can describe how changing resistor values can affect the voltage drop experienced			
I can design a potential divider circuit to perform a certain task			
I can compare the differences between primary and secondary cells			
I can describe the mechanics required to recharge a battery			
I can define the electromotive force and describe how it is different than the battery's voltage			
I can solve for a circuit that includes a battery with internal resistance			
I can describe how a battery's voltage changes over time			

# 8 | Electricity

## Shelving Guide

### Charge

Symbol	<b>q</b>	Unit	Coulombs [C]
Charge of 1 Electron		$1.6 \times 10^{-19} \text{ C}$	
# of Electrons per Coulomb		$6.25 \times 10^{18} \text{ e}^-$	

### Current

Symbol	<b>I</b>	Unit	Amperes [A]
Unit in terms of Coulombs		$A = \frac{C}{s}$	

### Drift Speed

	Variable Symbol	Unit
Current	<b>I</b>	<b>A</b>
# of Electrons per $\text{m}^3$	<b>n</b>	---
Cross Sectional Area	<b>A</b>	<b><math>\text{M}^2</math></b>
Drift Speed	<b>v</b>	<b><math>\text{m s}^{-1}</math></b>
Charge	<b>q</b>	<b>C</b>

Data Booklet Equation:

$$I = nAvq$$

Cross Sectional Area:

$$A = \pi r^2$$

### Electrical Properties

Property	What is it?	Symbol	Unit
Voltage	Potential Difference	<b>V</b>	Volts [V]
Current	The rate at which charges move through a wire	<b>I</b>	Amperes [A]
Resistance	How hard it is for a current to flow through a conductor	<b>R</b>	Ohms [ $\Omega$ ]

### Kirchhoff's Laws

$\Sigma I = 0$ (junction)				$\Sigma V = 0$ (loop)			
The total current coming into a junction must equal the total current leaving the same junction				The sum of the voltages (potential differences) provided must equal the voltages dissipated across components			
				Across resistors		Always Negative	
Entering Junction	$\rightarrow$	$\bullet$	Positive	Negative to Positive	$\rightarrow$	$\text{  }$	Positive
Exiting Junction	$\bullet$	$\rightarrow$	Negative	Positive to Negative	$\rightarrow$	$\text{  }$	Negative

## Ohm's Law

	$V = I \times R$	<b>Ohmic Resistor</b> 	<b>Non-Ohmic Resistor</b> 
	$I = \frac{V}{R}$		
	$R = \frac{V}{I}$		

## Equivalent Resistance

	Drawing with $R_1$ and $R_2$	Equation
Series		$R_{total} = R_1 + R_2 + \dots$
Parallel		$\frac{1}{R_{total}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$

## Measuring Circuits

	Ammeter	Voltmeter
Ideal Resistance	$R = 0 \Omega$	$R = \infty \Omega$
How is it connected to the component being measured?	Ammeters must be connected in <b>series</b>	Voltmeters must be connected in <b>parallel</b>
Drawing of meter measuring $R_1$		

## Resistivity

	Variable Symbol	Unit
Resistivity	$\rho$	$\Omega \text{ m}$
Resistance	$R$	$\Omega$
Cross Sectional Area	$A$	$\text{m}^2$
Length	$L$	$\text{m}$

Data Booklet Equation:

$$\rho = \frac{RA}{L}$$




Cross Sectional Area:

$$A = \pi r^2$$

## Power

In terms of V and I	In terms of I and R	In terms of V and R
$P = V \times I$	$P = I^2 R$	$P = \frac{V^2}{R}$

## Voltage Dividers

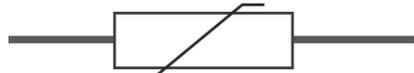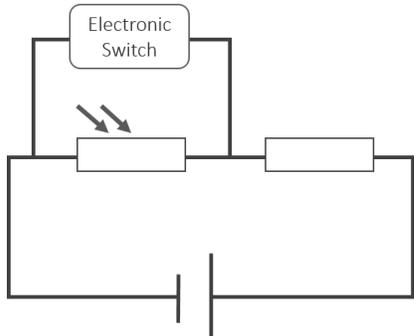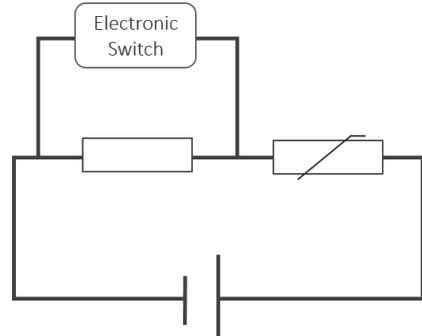	Light-Dependent Resistor	Thermistor
Symbol		
Relationship	Light Increases	Heat Increases
	Resistance <b>Decreases</b>	Resistance <b>Decreases</b>
Circuit	<p>Switch turns on in the dark:</p> 	<p>Switch turns on in a fire:</p> 

## Batteries

Primary Cells	Secondary Cells
<i>Cannot be recharged</i>	<i>Can be recharged by passing a current through the battery in the opposite direction as it would normally travel</i>

	Variable Symbol	Unit
Electromotive Force (e.m.f)	$\epsilon$	V
Current	$I$	A
Circuit Resistance	$R$	$\Omega$
Internal Resistance	$r$	$\Omega$

Data Booklet Equation:

$$\epsilon = I(R + r)$$